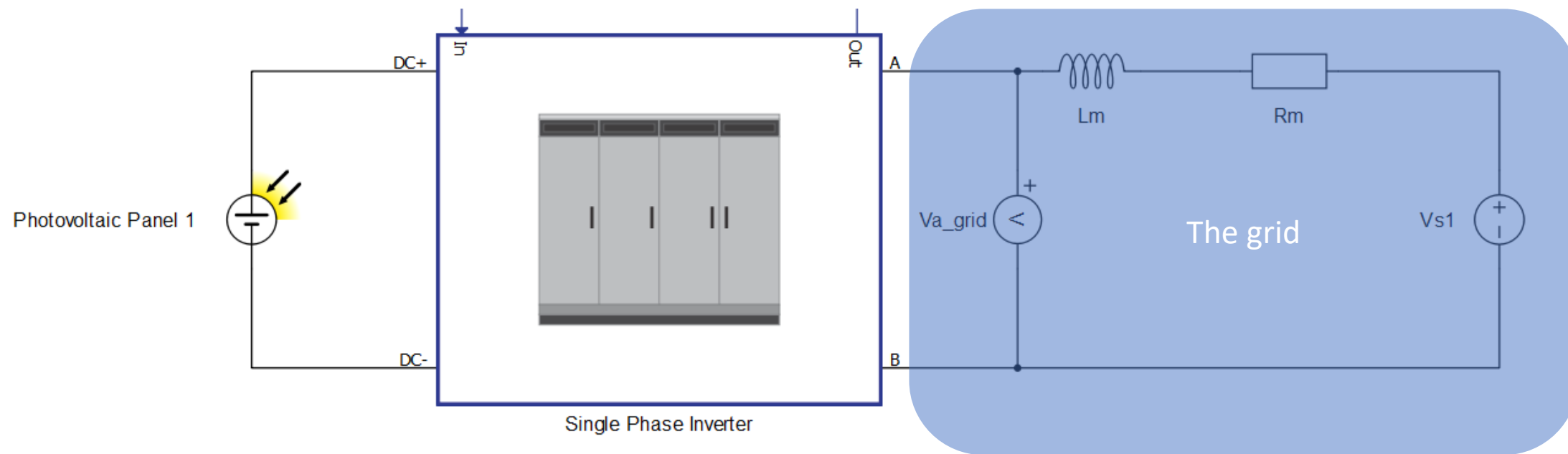


PV inverter control





Typhoon HiL implementation explanation

The plant






Model of PV panels

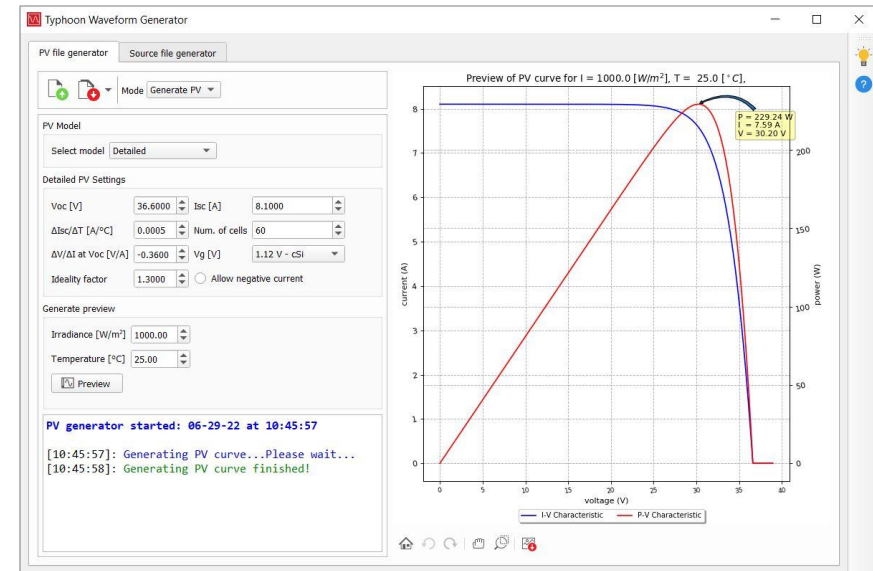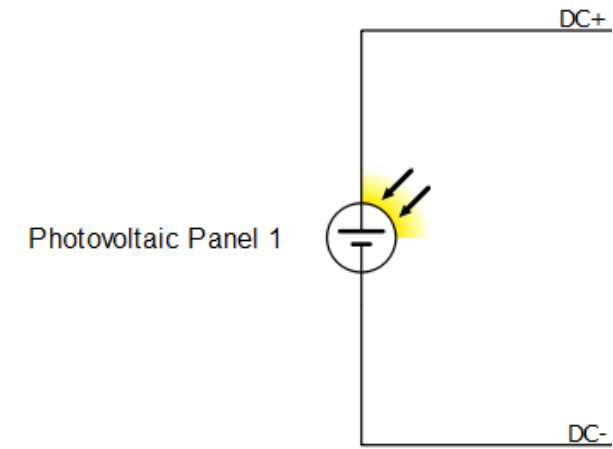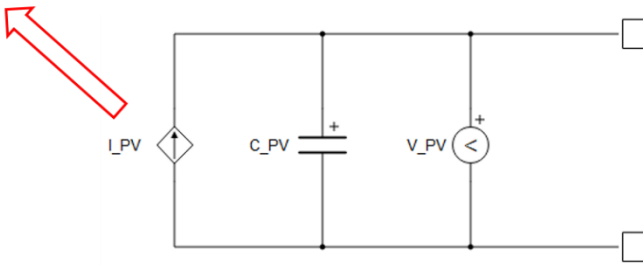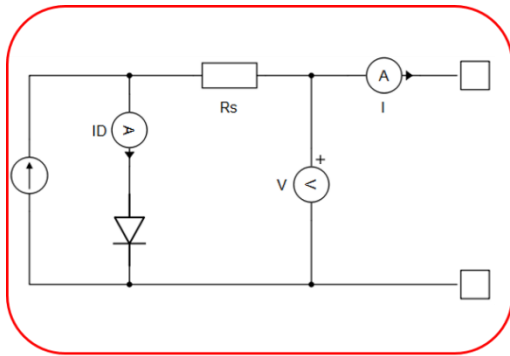- Classical current source + diode model
- Models the I-V curve



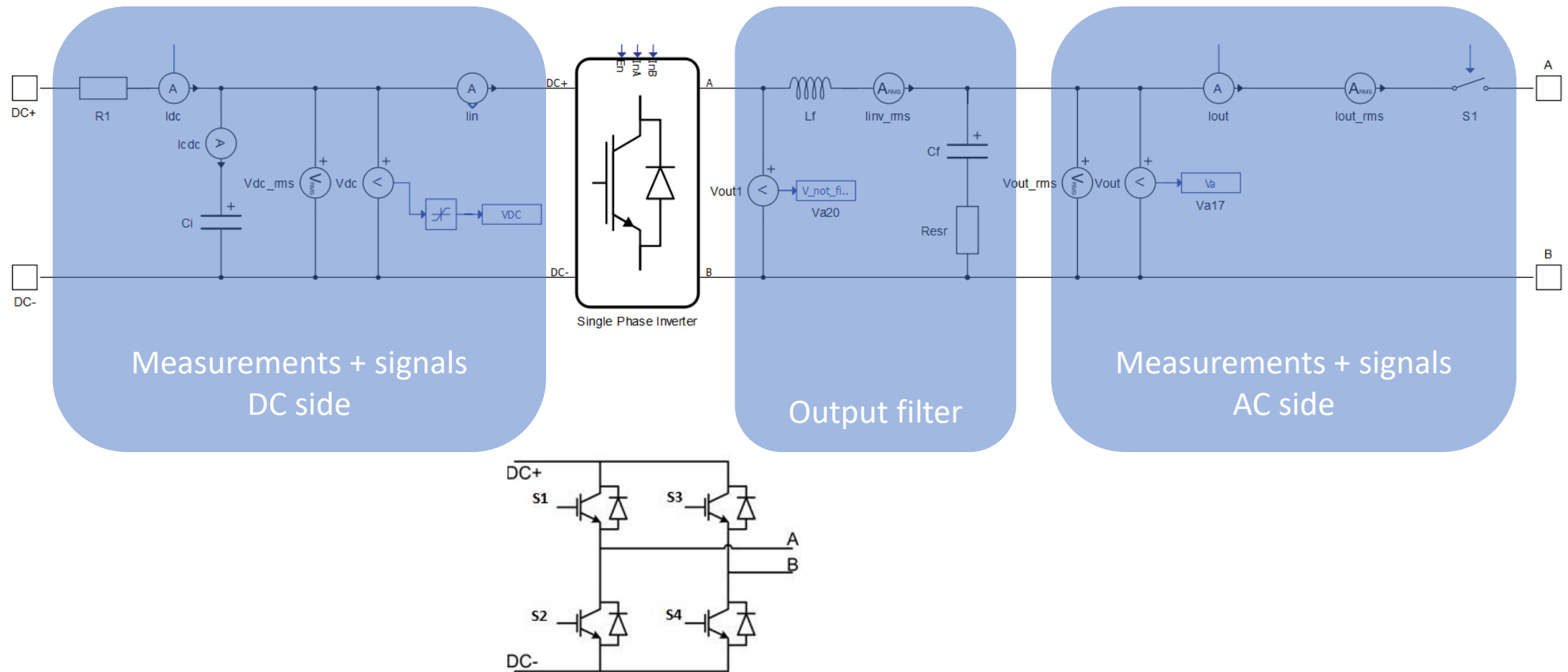Let's dive into the inverter – electrical part




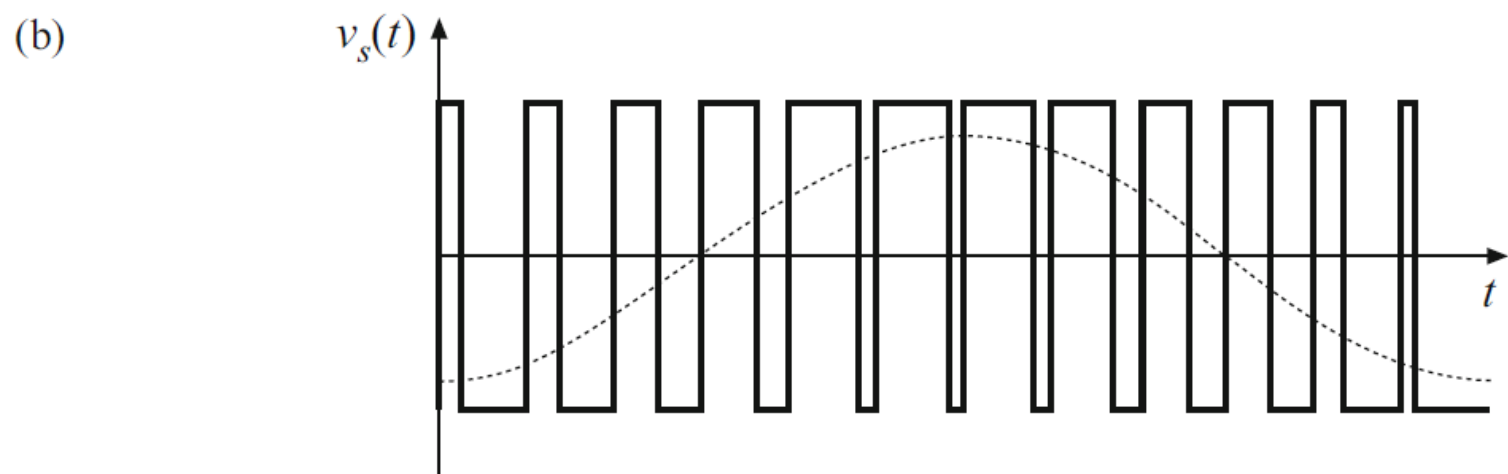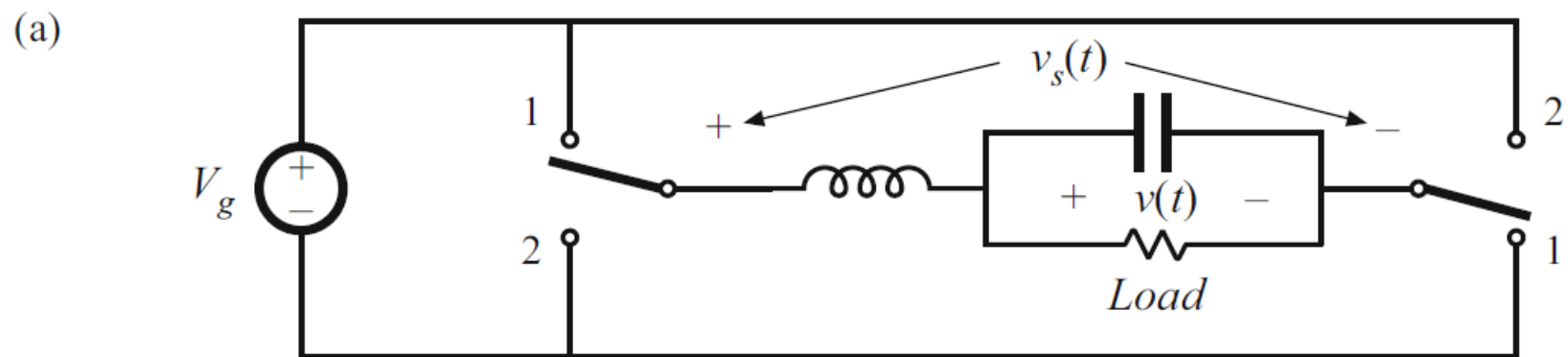


Let's dive into the inverter - control

- How is the inverter controlled?
 - This is a grid-following converter
 - It thus requires active and reactive setpoints P_{ref} and Q_{ref}
 - P_{ref} is obtained from MPPT, relatively slow control loop
 - Q_{ref} is set by the user here, but could be the result of a voltage droop controller
 - It « reads » network voltage V_A -> for reference
 - It « reads » the network current I_a -> for feedback control
 - It generates the signal to modulate the switches so as to produce the right I_a , in amplitude and phase.
 - This is a fast control loop
 - Accounting for the limits of the inverter (S_a)

MPPT control

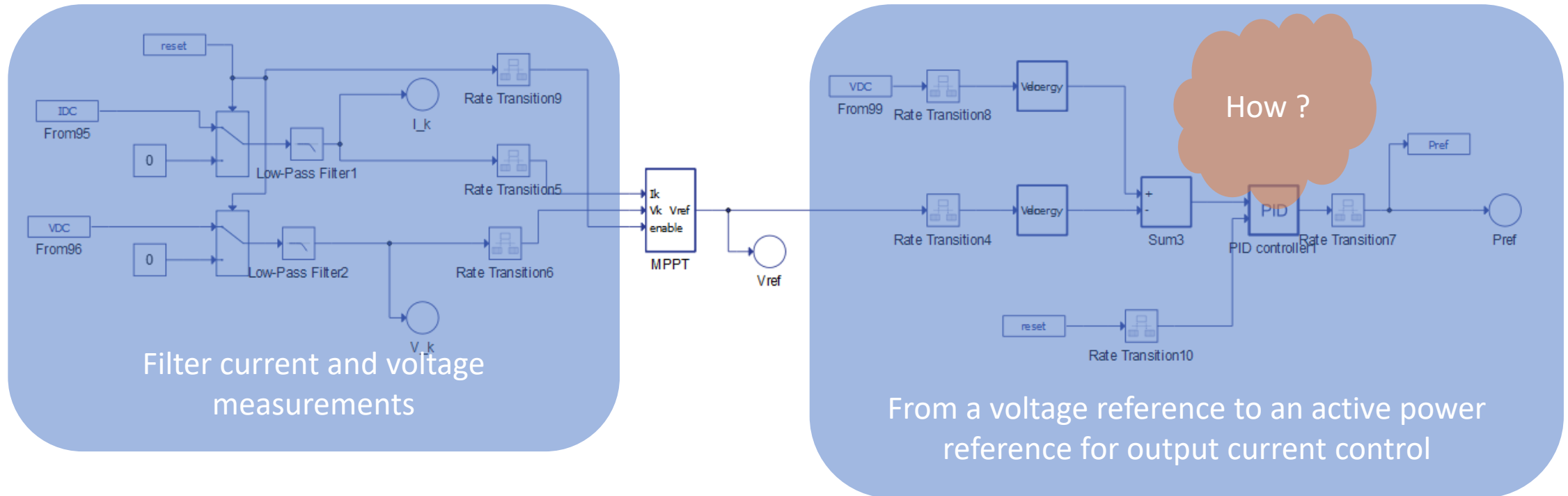

Current control

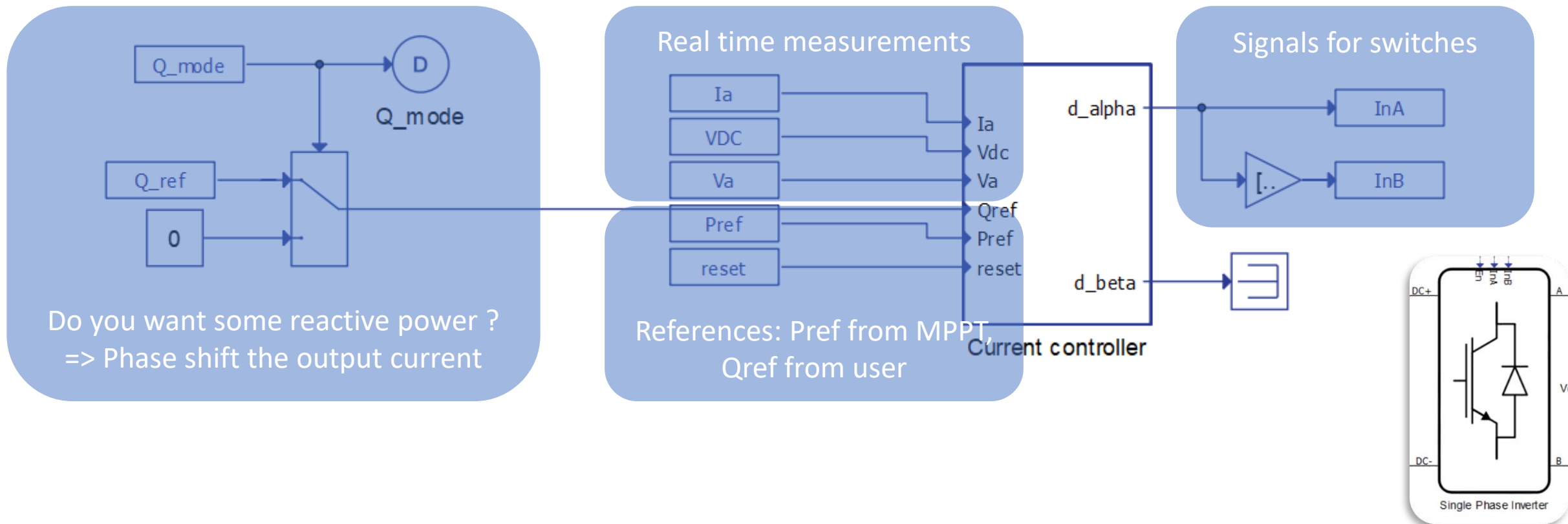

Current controller – Single phase dq current control algorithm

Phase lock loop + dq transform \Rightarrow measure the voltage frequency, project the voltage on d and q axes, provide a phase reference for the current



DQ transform for the current


dq transform

- Instead of working with instantaneous values that change all the time, apply a transformation to obtain important information for control:
 - How is the grid current phasor placed with respect to voltage phasor
 - “Kind of equivalent to working in DC”
- The dq transform is the composition of the Clarke and Park transforms
 - Clarke transform: “Encode time-varying values on fixed $\alpha - \beta$ axes (2D)”
 - Park transform: Let the axes rotate to “get rid of the $e^{j\omega t}$ ”
- See for instance: O’Rourke, C. J., Qasim, M. M., Overlin, M. R., & Kirtley, J. L. (2019). A Geometric Interpretation of Reference Frames and Transformations: Dq0, Clarke, and Park. *IEEE Transactions on Energy Conversion*, 34(4), 2070–2083. <https://doi.org/10.1109/TEC.2019.2941175>


Phase Lock Loop (PLL)

- The dq transform requires
 - a grid angle
- This is obtained using a PLL block (phase lock loop)
- Outputs the grid frequency as a by-product.
- dq and PLL blocks can be intertwined:



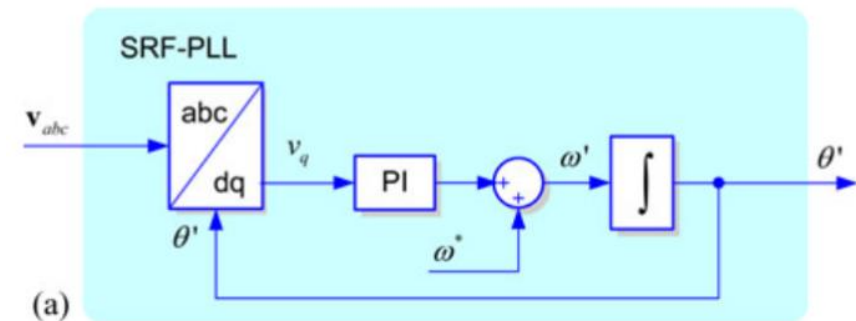
See Rocabert, J., Luna, A., Blaabjerg, F., & Rodríguez, P. (2012). Control of power converters in AC microgrids. *IEEE Transactions on Power Electronics*, 27(11), 4734–4749. <https://doi.org/10.1109/TPEL.2012.2199334>



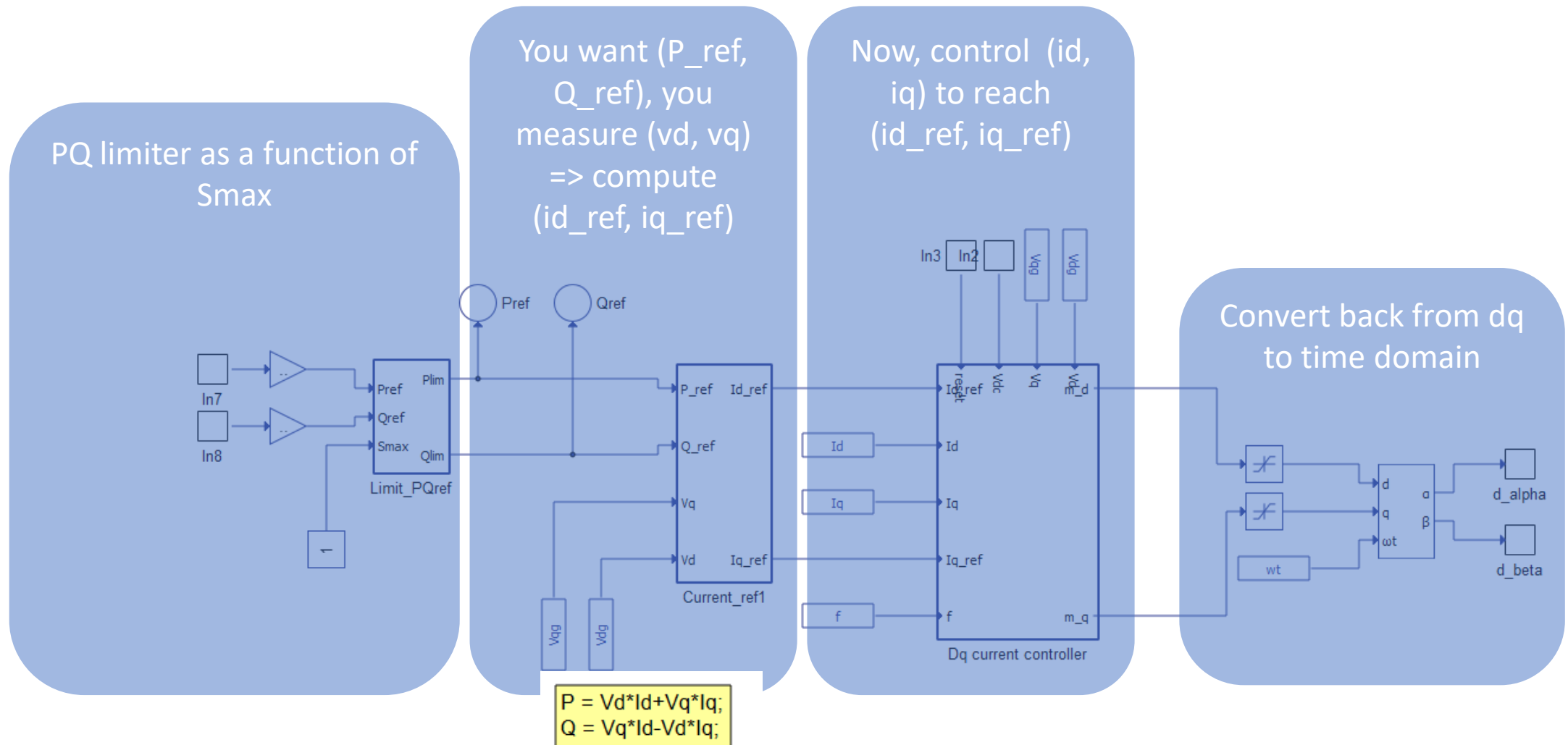Current controller – Single phase dq current control algorithm



DQ Current controller

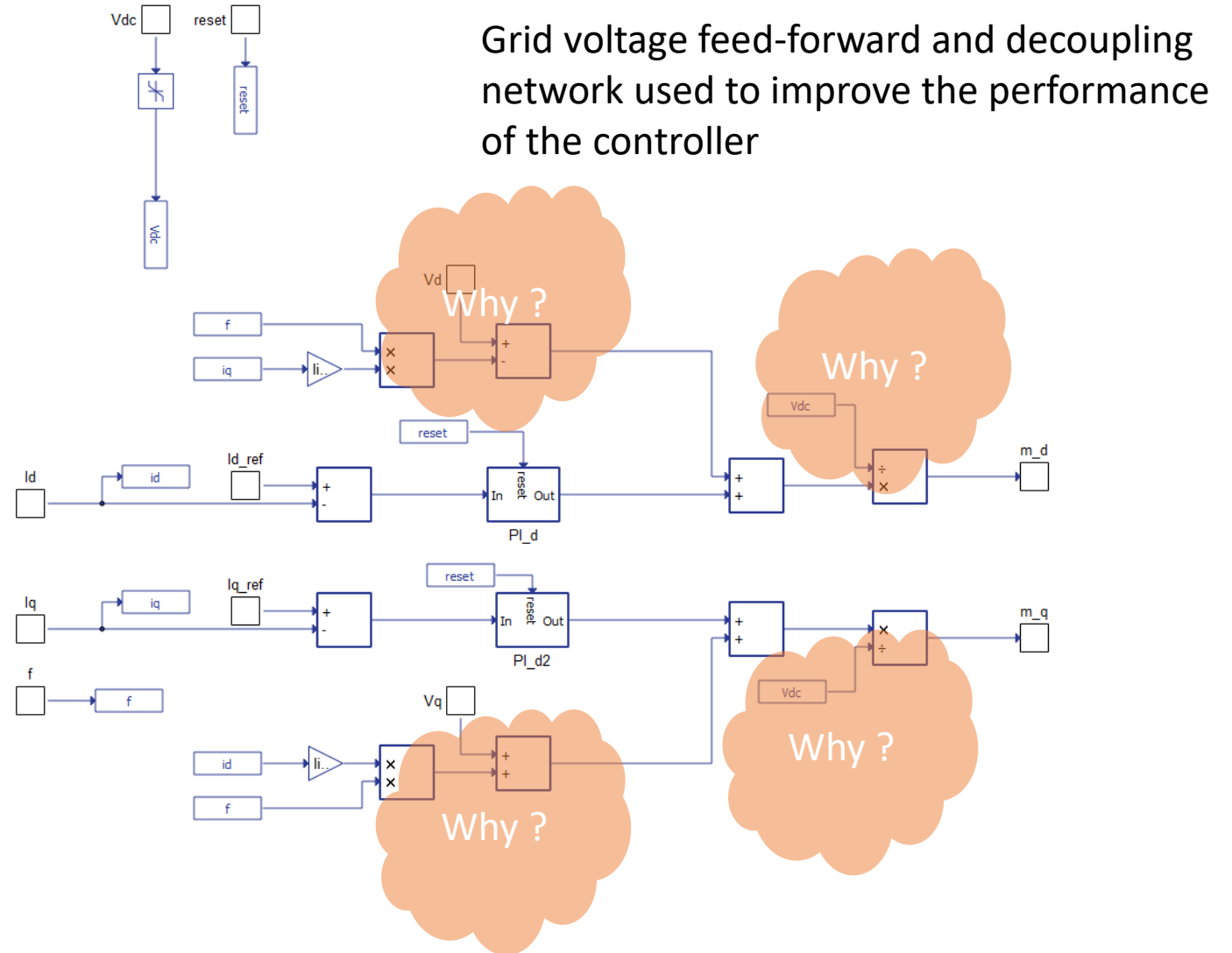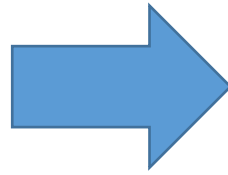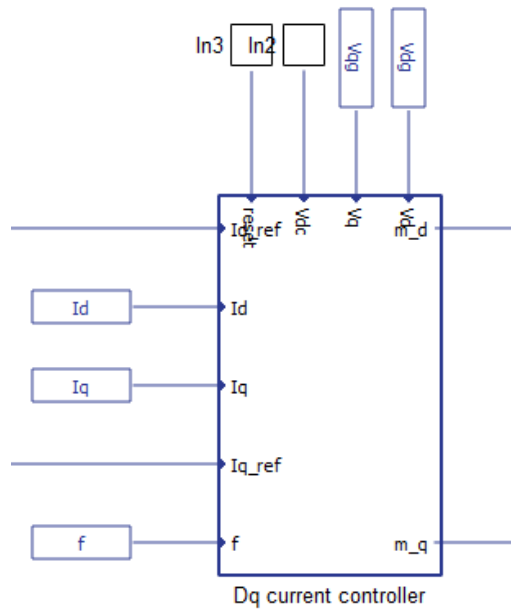

Power measurement

